




BITS Pilani
Pilani Campus

Mechatronics AEZG511

Lecture

Signal conditioning

Data Acquisition system

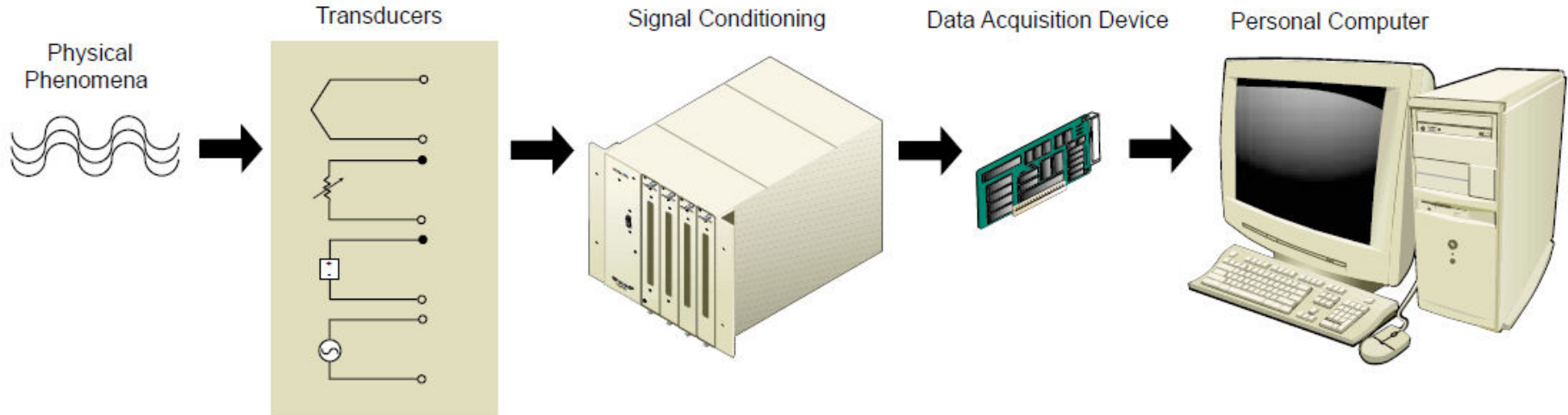

Operational Amplifiers (Op Amps)

Why Study Amplification?




[1]

- Sensor signals are in millivolts or milliamps
- The analog front end for a sensor is more complex than the digital control circuitry for the sensor-actuator loop
- The main issues for sensor interfaces are accuracy, noise, offset, drift, and impedance
- All of these issues come back to amplification

Symbol (Each Amplifier)





Ideal Op Amp

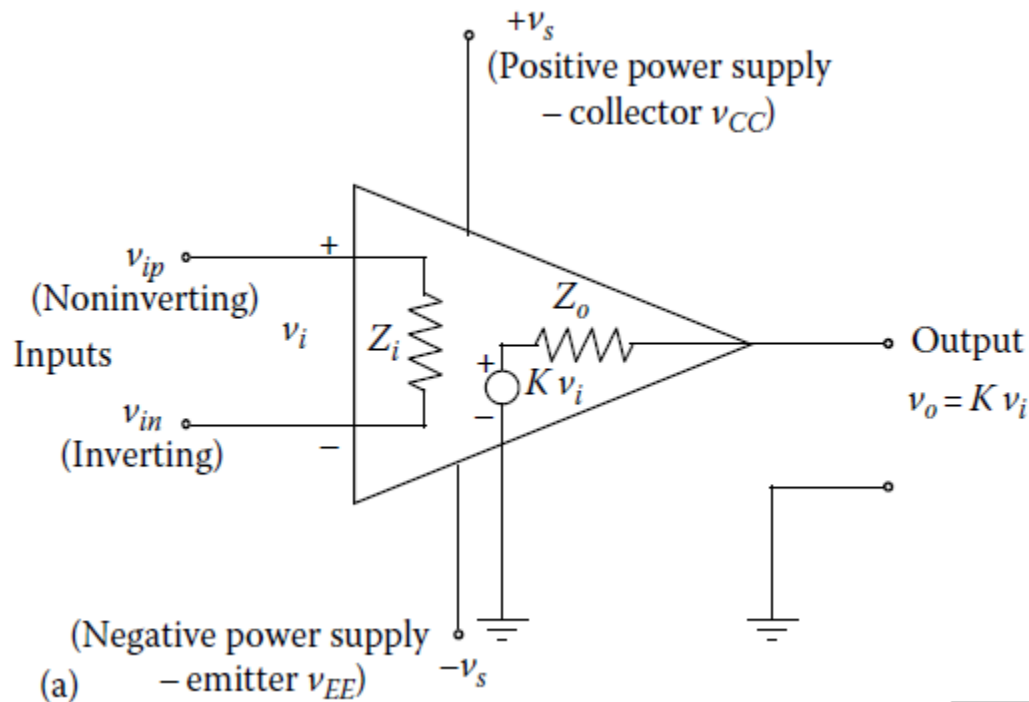

V_i - The difference in voltage between Non Inv and Inv inputs


K - Output gain (10^5 to 10^7)

  


Pin designations:

- 1 Offset null
- 2 Inverting input
- 3 Noninverting input
- 4 Negative power supply v_{EE}
- 5 Offset null
- 6 Output
- 7 Positive power supply v_{CC}
- 8 NC (not connected)




Internal Circuitry of Op Amp 741

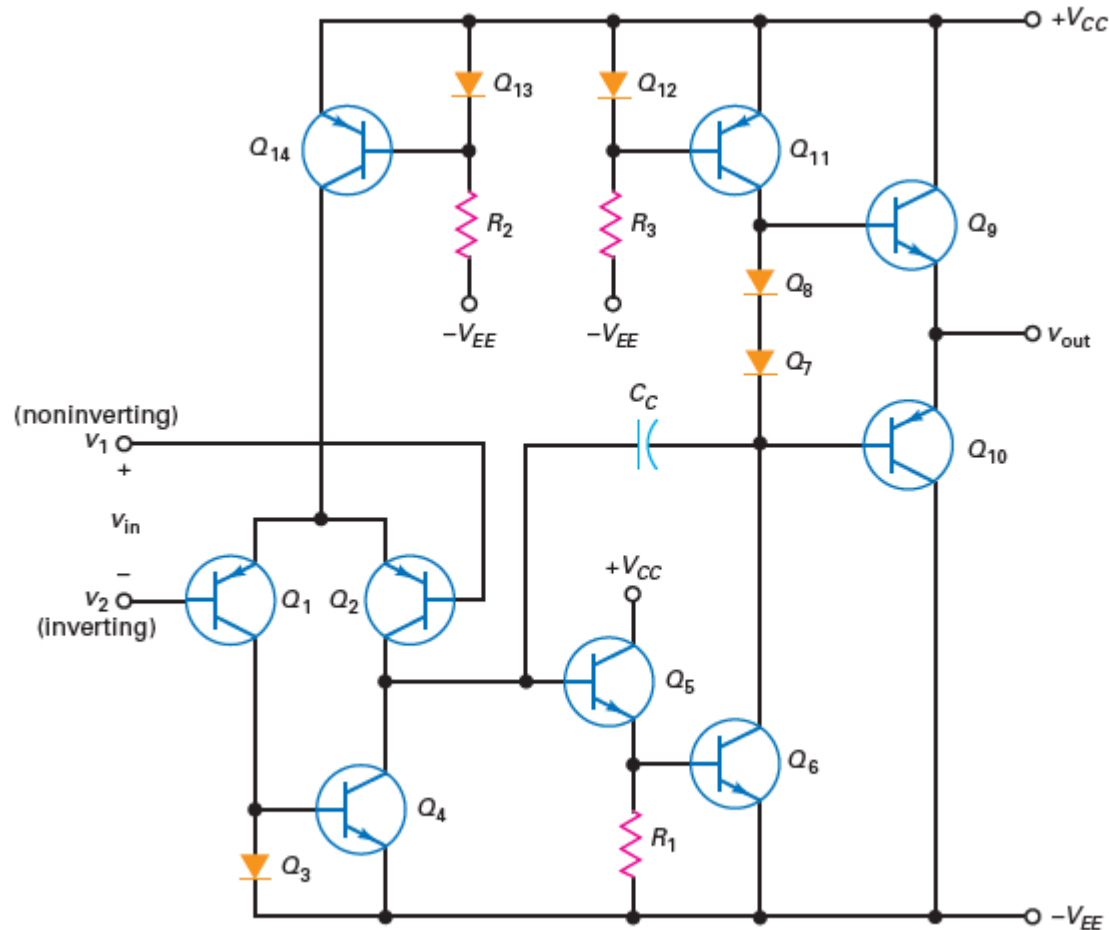

Typical Characteristics of Op amp

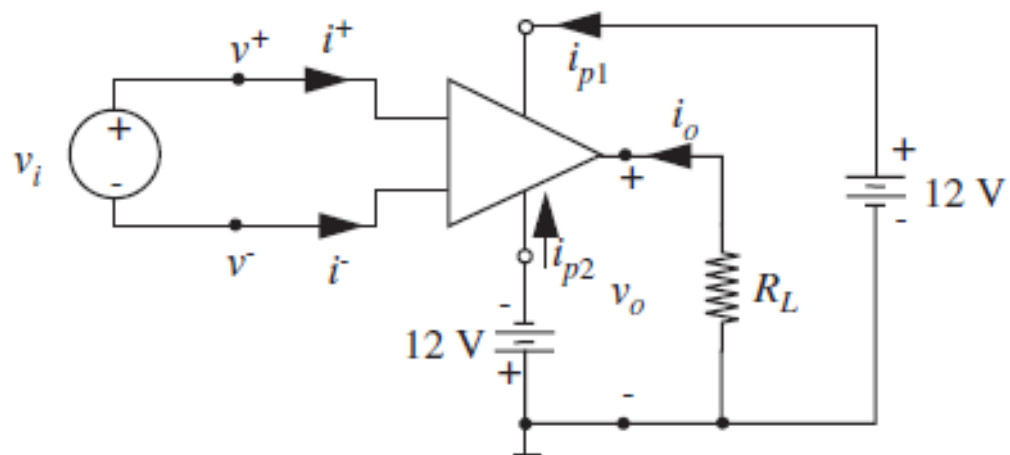


(a)

   

Ideal Op Amp

| PARAMETER NAME | PARAMETERS SYMBOL | VALUE |
|----------------------|-------------------|----------|
| Input current | I_{IN} | 0 |
| Input offset voltage | V_{OS} | 0 |
| Input impedance | Z_{IN} | ∞ |
| Output impedance | Z_{OUT} | 0 |
| Gain | K | ∞ |

 

$$v_o = K v_i$$

Simplified diagram showing only voltage inputs (without external power supply)

Ideal Op Amp

$$v_o = Kv_i$$




$$v_i = v_{ip} - v_{in}$$

If V_{in} is ground ; $v_o = Kv_{ip}$


If V_{ip} is ground; $v_o = -Kv_{in}$

This is why V_{in} is called Non- Inverting
and

V_{ip} is called Inverting input

   

Virtual Ground of Op Amp

 

This assumption of Virtual Ground saves us from lots of algebraic manipulations!!!

+ terminal is connected to ground

Gain (K) of amplifier is 100,000

Output voltage is say 10 V

Means input voltage is 0.0001.

This can be considered **as Zero!!**

Point X is at "0" Voltage!!

Called Virtual Ground

Ideal Op Amp Assumptions(Summarized)

Input Impedance is Very High (10 Mega Ohms)


Output Impedance is Very low (10 Ohms)

No current passes through Op amp

Virtual ground assumption can be made safely

Gain is very high (100,000 – 1,000,000)

Inverting amplifier

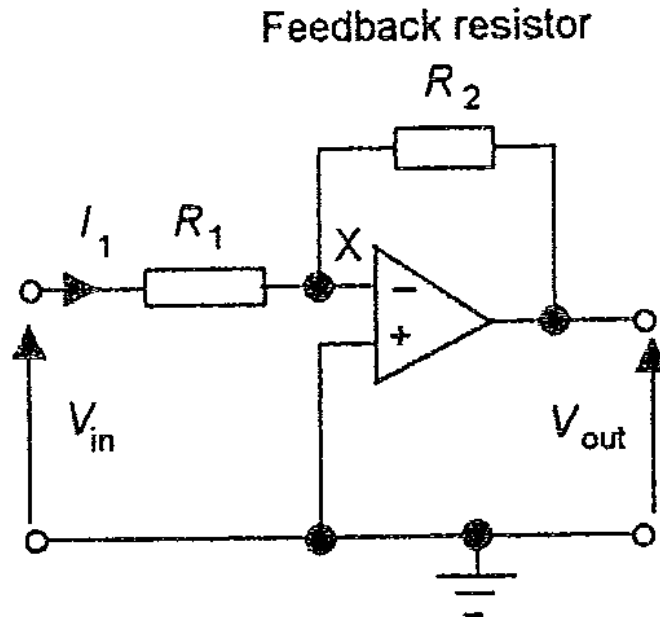

Potential difference across R_1 is

$$V_{in} - V_x = I_1 \times R_1$$

Potential difference across R_2 is

$$V_x - V_{out} = I_2 \times R_2$$


No current can flow through X into Op Amp (Refer our assumptions)

$$\text{Means } I_1 = I_2$$

Again $V_x = 0$ (based on virtual ground)

$$\text{Voltage gain of circuit} = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Non – Inverting amplifier

 

This is voltage divider circuit

R_2 and R_1 are in series with X in between.


$$V_X = \frac{R_1}{R_1 + R_2} V_{out}$$

Again $V_X = V_{in}$ (No current flows through Op Amp)

$$\text{Voltage gain of circuit} = \frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$


Voltage Follower

 Non Inverting amplifier without resistors is a follower



- a) Used in voltage divider circuit
- b) As isolators

Summing Amplifier

 

$$I = I_A + I_B + I_C$$

$$-\frac{V_{out}}{R_2} = \frac{V_A}{R_A} + \frac{V_B}{R_B} + \frac{V_C}{R_C}$$

$$V_{out} = -\left(\frac{R_2}{R_A}V_A + \frac{R_2}{R_B}V_B + \frac{R_2}{R_C}V_C\right)$$


If $R_A = R_B = R_C = R_1$ then

$$V_{out} = -\frac{R_2}{R_1}(V_A + V_B + V_C)$$

How to generate average of these signals????

Integrating Amplifier

 Replace resistor R2 in inverting amplifier with a capacitor



Interchange the capacitor and Resistor positions you get **Differentiating Amplifier** – **Verify!!!!**

$$q = Cv,$$

$$i = dq/dt = C dv/dt.$$

$$\frac{v_{in}}{R} = -C \frac{dv_{out}}{dt}$$


Rearranging this gives

$$dv_{out} = -\left(\frac{1}{RC}\right) v_{in} dt$$

Integrating both sides gives

$$v_{out}(t_2) - v_{out}(t_1) = -\frac{1}{RC} \int_{t_1}^{t_2} v_{in} dt$$

Differencing amplifier

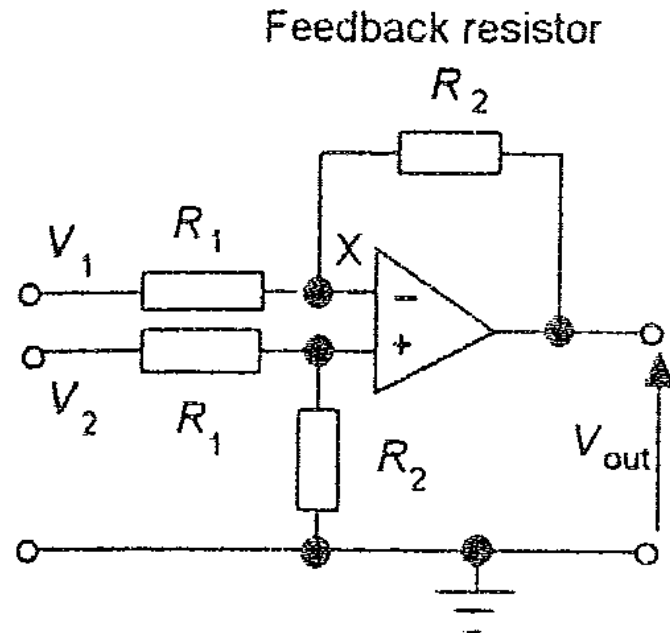


$$\frac{V_X}{V_2} = \frac{R_2}{R_1 + R_2}$$

$$\frac{V_1 - V_X}{R_1} = \frac{V_X - V_{out}}{R_2}$$

$$\frac{V_{out}}{R_2} = V_X \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{V_1}{R_1}$$



At same Potential !

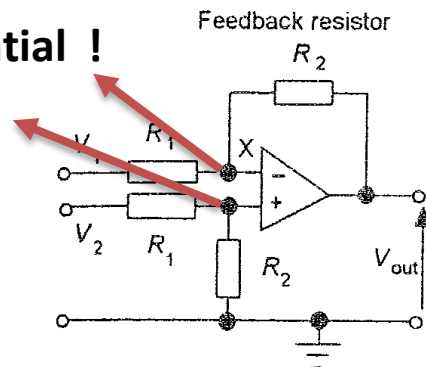


Hence substituting for V_X using the earlier equation,

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

Voltage Comparator

  


Logarithmic amplifier

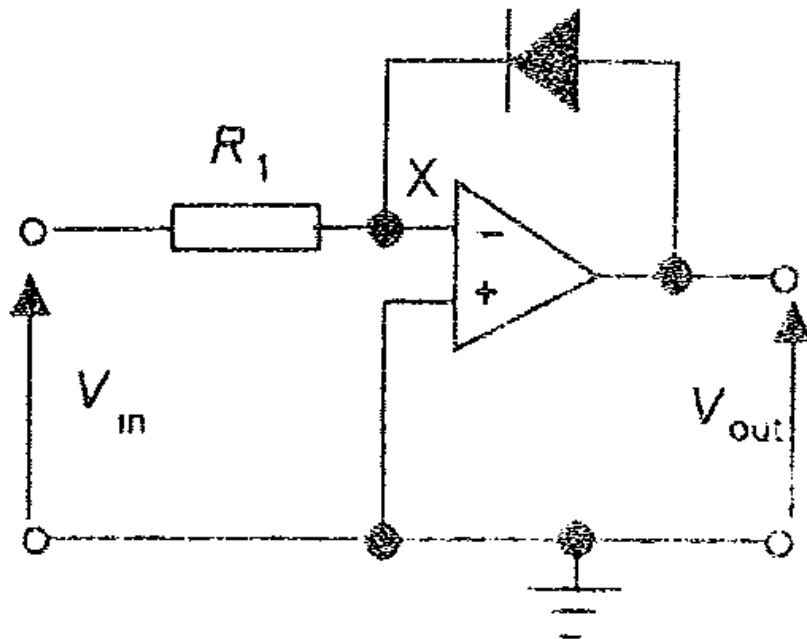


Linearizes exponential signals

Amplifier errors

 

Sliding contact of the potentiometer to a negative supply, so that V_{out} is zero, when V_+ and V_- are equal

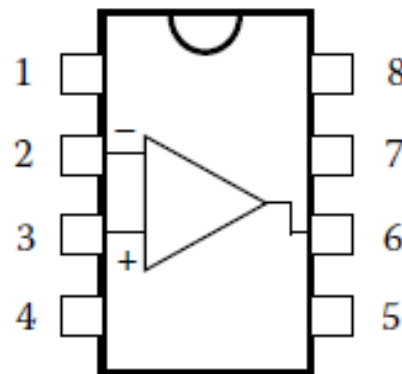Offset voltage: Presence of output even if v^+ and v^- are shorted



Pin designations:


- 1 Offset null
- 2 Inverting input
- 3 Noninverting input
- 4 Negative power supply v_{EE}
- 5 Offset null
- 6 Output
- 7 Positive power supply v_{CC}
- 8 NC (not connected)

Slew rate

 Example Slew Rate Calculation

Amplifier requirements: 25 kHz & peak voltage 5V

Slew rate = $2 \pi f V$
 = $2 \times 3 \times 25\,000 \times 5$
 = $750\,000 \text{ V / s}$
 = $0.75 \text{ V / } \mu\text{s}$







| | | | | | | | | | | |
|--------------------------------|---|-------|------|-----|----------|----------|--|----------|----------|------------------|
| | $R_L \geq 2 \text{ k}\Omega$ | | | | ± 10 | ± 13 | | ± 10 | ± 13 | |
| Output Short Circuit Current | $T_A = 25^\circ\text{C}$ | 10 | 25 | 35 | | 25 | | 25 | | mA |
| | $T_{\text{AMIN}} \leq T_A \leq T_{\text{AMAX}}$ | 10 | | 40 | | | | | | |
| Common-Mode Rejection Ratio | $T_{\text{AMIN}} \leq T_A \leq T_{\text{AMAX}}$ | | | | | | | | | |
| | $R_S \leq 10 \text{ k}\Omega, V_{\text{CM}} = \pm 12\text{V}$ | | | | 70 | 90 | | 70 | 90 | dB |
| | $R_S \leq 500\Omega, V_{\text{CM}} = \pm 12\text{V}$ | 80 | 95 | | | | | | | |
| Supply Voltage Rejection Ratio | $T_{\text{AMIN}} \leq T_A \leq T_{\text{AMAX}}$ | | | | | | | | | |
| | $V_S = \pm 20\text{V to } V_S = \pm 5\text{V}$ | | | | | | | | | |
| | $R_S \leq 500\Omega$ | 86 | 96 | | | | | | | dB |
| | $R_S \leq 10 \text{ k}\Omega$ | | | | 77 | 96 | | 77 | 96 | |
| Transient Response | $T_A = 25^\circ\text{C}, \text{Unity Gain}$ | | | | | | | | | |
| Rise Time | | | 0.25 | 0.8 | | 0.3 | | 0.3 | | μs |
| Overshoot | | | 6.0 | 20 | | 5 | | 5 | | % |
| Bandwidth ⁽²⁾ | $T_A = 25^\circ\text{C}$ | 0.437 | 1.5 | | | | | | | MHz |
| Slew Rate | $T_A = 25^\circ\text{C}, \text{Unity Gain}$ | 0.3 | 0.7 | | | 0.5 | | 0.5 | | V/ μs |
| Supply Current | $T_A = 25^\circ\text{C}$ | | | | 1.7 | 2.8 | | 1.7 | 2.8 | mA |
| Power Consumption | $T_A = 25^\circ\text{C}$ | | | | | | | | | |
| | $V_S = \pm 20\text{V}$ | | 80 | 150 | | | | | | mW |
| | $V_S = \pm 15\text{V}$ | | | | 50 | 85 | | 50 | 85 | |

Slew rate often measured in Volts / microsecond



(2) Calculated value from: BW (MHz) = 0.35/Rise Time (μs).

Protectors

Zener Diode (Voltage Regulator)

    

Zener circuit design calculation

  

Given,

$V_S = 20 \text{ Volt to } 24 \text{ Volt}$

$V_L = 12 \text{ Volt}$

$R_L = 24 \text{ Ohms}$

Select **Zener**

$V_Z = ?$ $I_Z = ?$ Power = ??

Zener voltage V_Z should be 12 Volts

Load current $= V_L / R_L = 12 / 24 = 500 \text{ mA}$

$R_S = (V_S - V_Z) / I_L = (20 - 12) / 500 \text{ mA} = 16 \text{ Ohms}$

Load current through resistor

$I_S (\text{max}) = (24 - 12) / 16 = 750 \text{ mA}$

$I_S (\text{min}) = (20 - 12) / 16 = 500 \text{ mA}$

$I_S = I_Z + I_L$

$750 = I_Z + 500 \text{ mA}$


$I_Z = 250 \text{ mA}$

Power of Zener $= 12 \text{ V} * 250 \text{ mA} = 3 \text{ Watts}$


Suppose by chance voltage at source drops to 19 Volts, what will happen?

Zener Calculation (Home work)

 
If the Zener diode below is of 10 V breakdown then, what is V_{out} and Max Zener, min Zener currents




Zener Circuit

 


Opto Isolator

 

 Current from the source signal passes through the input LED which emits an infra-red light whose intensity is proportional to the electrical signal.




21842


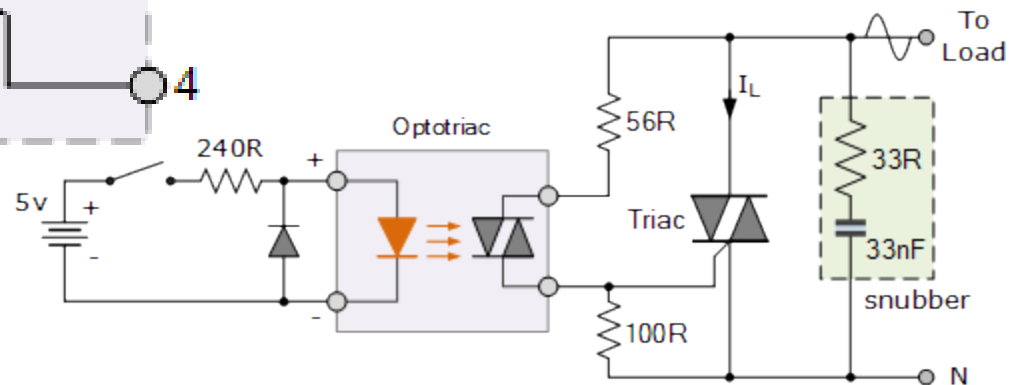


- Isolation test voltage 5000 V_{RMS}

Protection Circuit

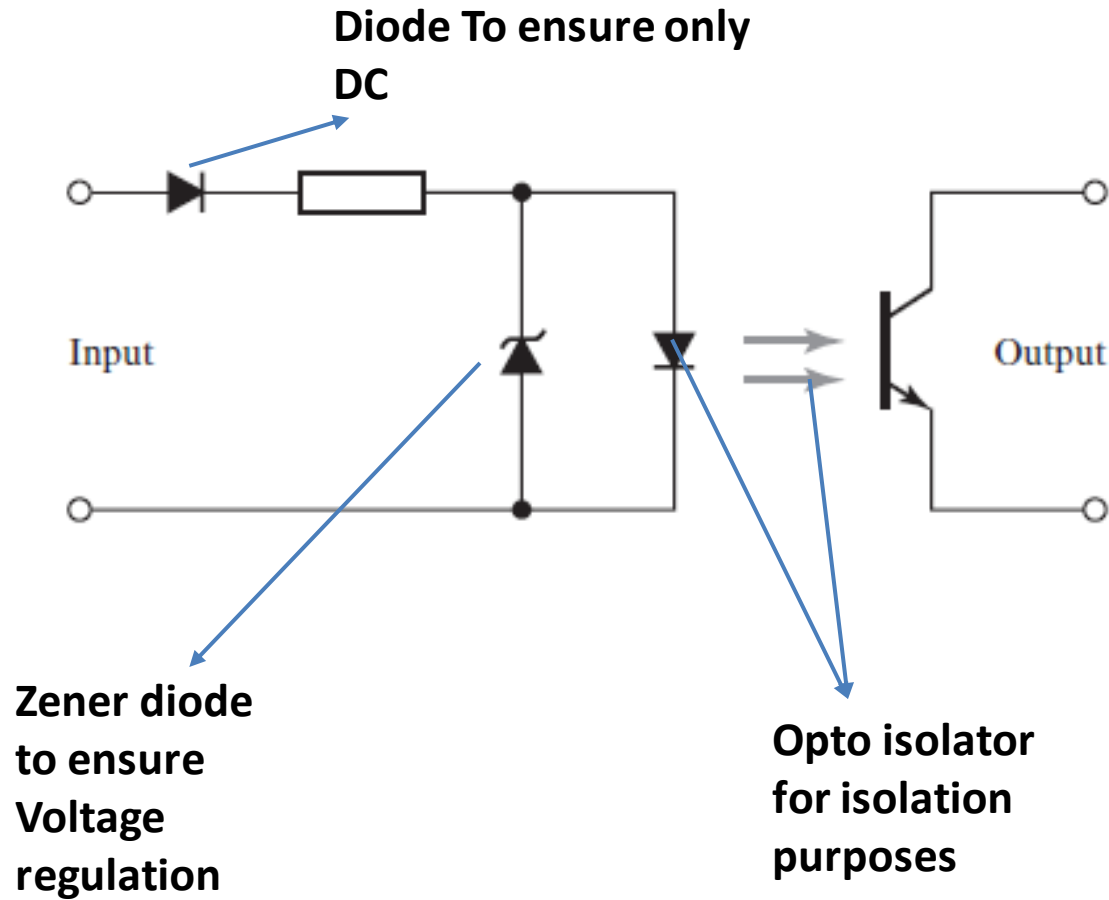

Wheatstone bridge

 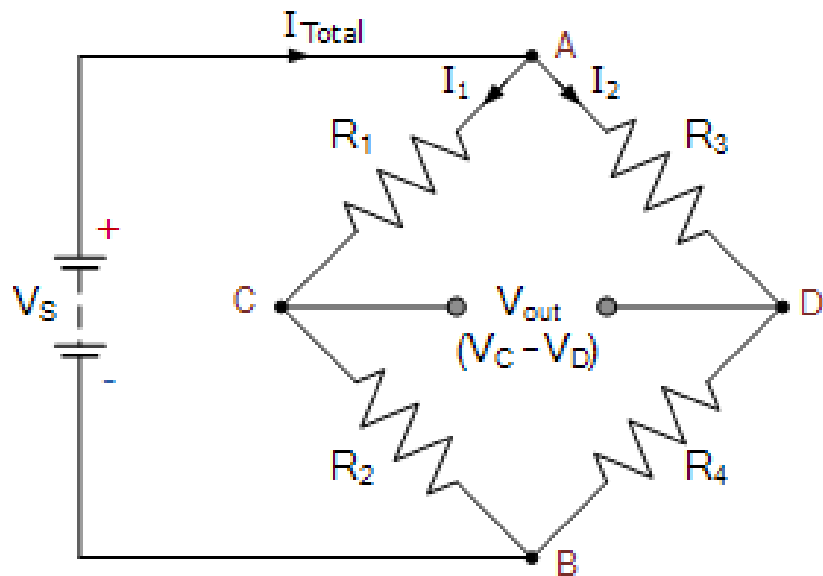


The above circuit is balanced as $V_C = V_D$


As

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Wheatstone bridge

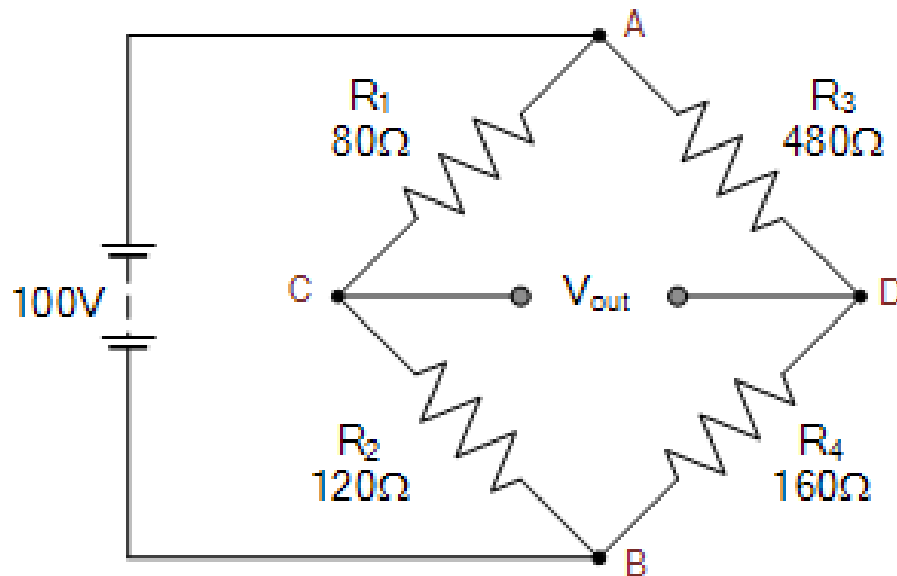


Unbalanced circuit
 V_c ? V_d ?

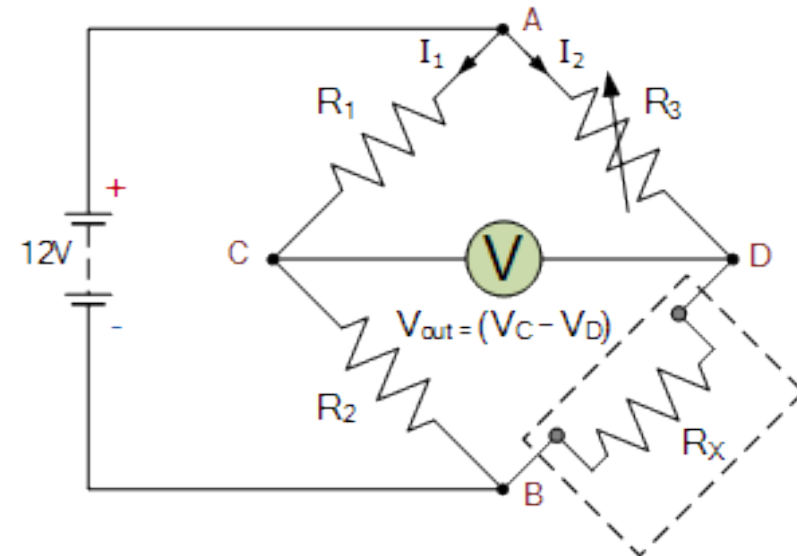

Connecting a RTD or strain
 gauge

Wheatstone bridge

 

Pass filters configurations


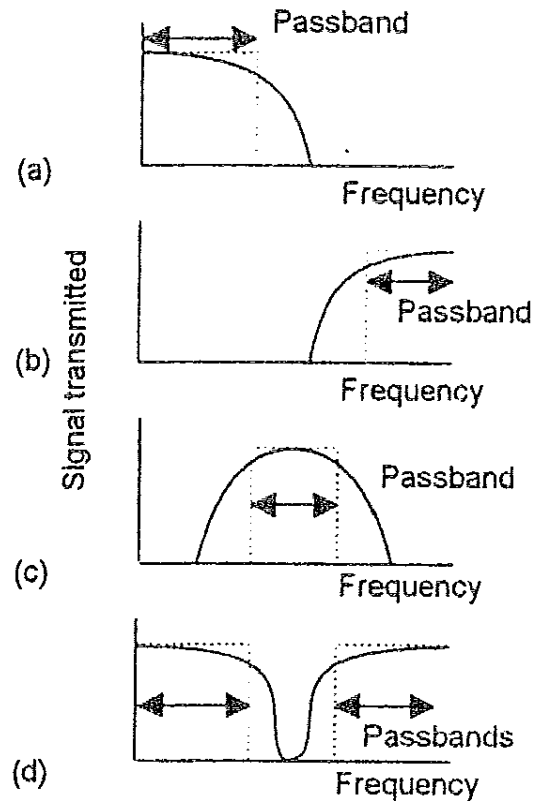


Fig. 3.19 Characteristics of ideal filters: (a) low pass, (b) high pass, (c) band pass, (d) band stop

Low pass filters

$$X_C = 1/2\pi fC.$$

 


$$\frac{V_{OUT}}{V_{IN}} = - \frac{X_C \parallel R_F}{R_G}$$

At very low frequencies $X_C \rightarrow \text{infinity}$ so R_F dominates the parallel combination in Equation and the capacitor has no effect. The gain at low frequencies is $-R_F/R_G$.

At very high frequencies $X_C \rightarrow 0$, so the feedback resistor is shorted out, thus reducing the circuit gain to zero (*The current flows through least resistance path, thereby offering making R_F redundant*)

High Pass filters

 


$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_F}{X_C \parallel R_G}$$

At very low frequencies $X_C \Rightarrow \infty$, so R_G dominates the parallel combination and the capacitor has no effect. The gain at low frequencies is $1 + R_F/R_G$. At very high frequencies $X_C \Rightarrow 0$, so the gain setting resistor is shorted out thus increasing the circuit gain to maximum.

Analog to Digital Digital to Analog Converters

Analog to Digital Schematic

 

Nyquist Theorem

When the signal is reconstructed from the samples, it is only when the sampling rate is at least twice that of the highest frequency in the analogue signal that the sample gives the original form of signal.

 


Fig. 3.29 Effect of sampling frequency: (a) analogue signal, (b) sampled signal, (c) sampled signal

A-D characteristics

MSB is a bit of the highest digit, and the LSB is a bit of the lowest digit

01100011



Conversion Rate: How many conversions per unit time

Voltage range: Reference voltage (Analog voltage that controller can handle)

Resolution :

$$\text{Voltage resolution} = \text{range}/2^n$$


n – number of bits

Quantization Error (Digitization accuracy)

Quantization error = Resolution Error / 2

Say a analog input of 5 V and we use 2 bit converter

 Means 0 0 , 0 1, 1 0 and 1 1 are the possible representation



Resolution: ?

Quantization error: ?

Calculation

Consider a thermocouple giving an output of $0.5 \text{ mV/}^\circ\text{C}$. What will be the word length required when its output passes through an analogue-to-digital converter if temperatures from 0 to 200°C are to be measured with a resolution of 0.5°C ? The full-scale output from the sensor is $200 \times 0.5 = 100 \text{ mV}$. With a word length n , this voltage will be divided into $100/2^n \text{ mV}$ steps. For a resolution of 0.5°C we must be able to detect a signal from the sensor of $0.5 \times 0.5 = 0.25 \text{ mV}$. Thus we require

$$0.25 = \frac{100}{2^n}$$

Hence $n = 8.6$. Thus a 9-bit word length is required.


Quantization Error (Digitization accuracy)

Determine the voltage resolution and digitization accuracy of an ideal 12-bit A/D converter with a 0 to 10 V range. Determine the output level if the input voltage is 6.5 V. Also, determine the corresponding analog input voltage at the following digital output values: 0 and 1000.

Solution:

From Equation (5.1), the voltage resolution of this A/D device is $10/2^{12} = 2.441$ mV. Thus, the digitization accuracy of the conversion is ± 1.220 mV.

Weighted resistor DAC

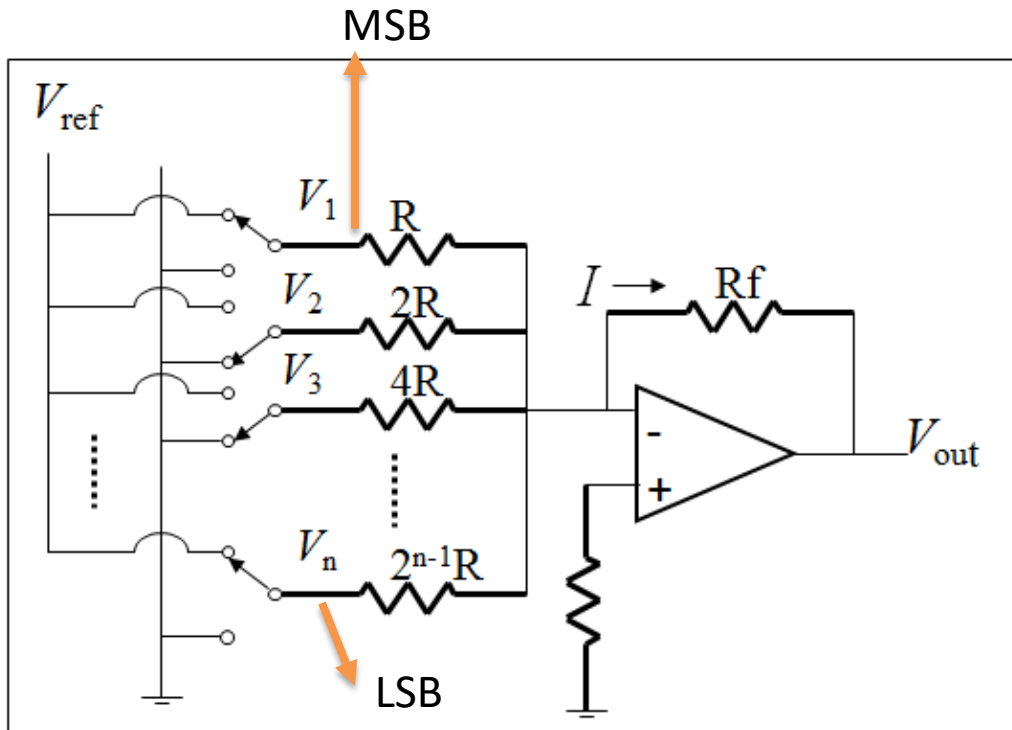


$$V_{out} = -IR_f = -R_f \left(\frac{V_1}{R} + \frac{V_2}{2R} + \frac{V_3}{4R} + \dots + \frac{V_n}{2^{n-1}R} \right)$$

The resistances are increased from MSB to LSB to adjust to the weightage of the binary digits


Availability of Accurate resistances is a problem and that too at varying temperatures, Limited to 4 bit conversions

R-2R Ladder DAC

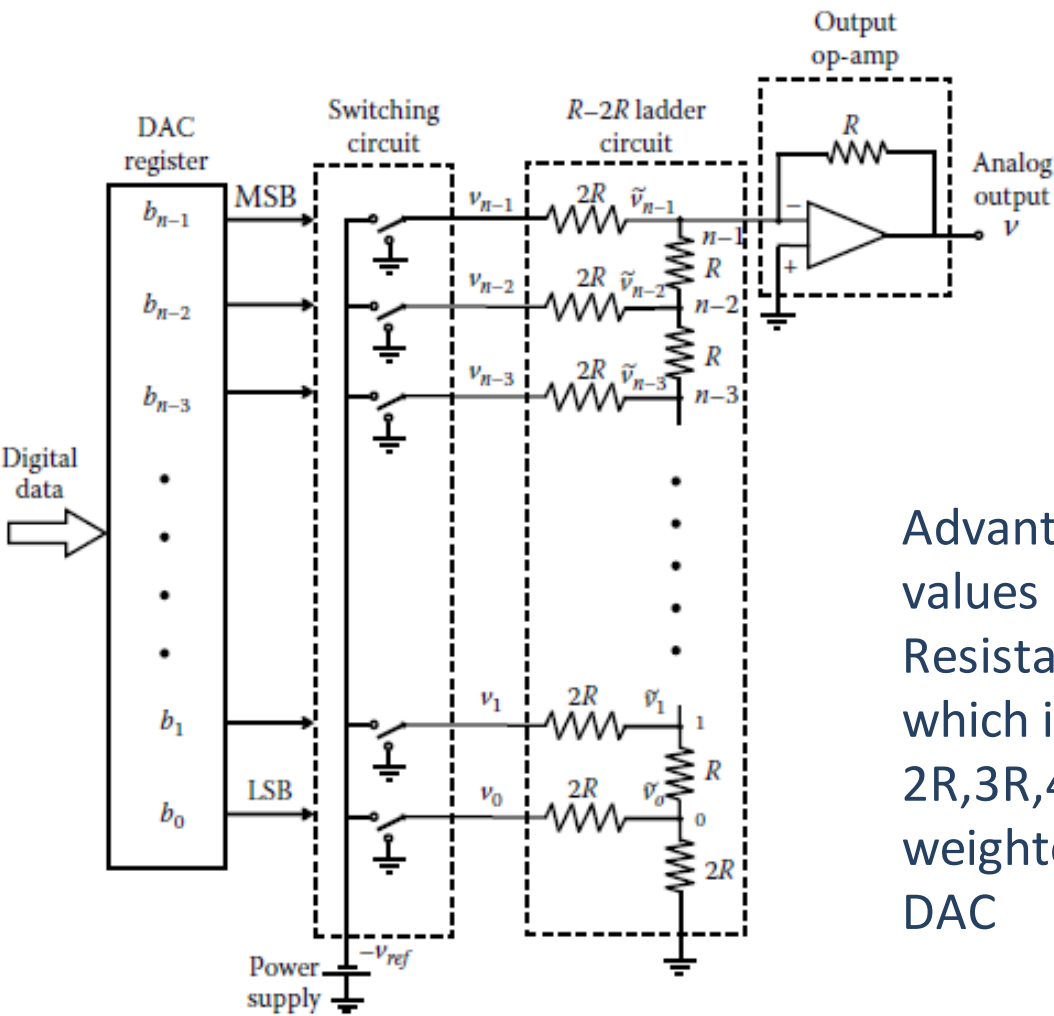

Advantage is only 2 values of Resistances are used which is better than 2R,3R,4R etc used in weighted resistor DAC



Sample and Hold circuit

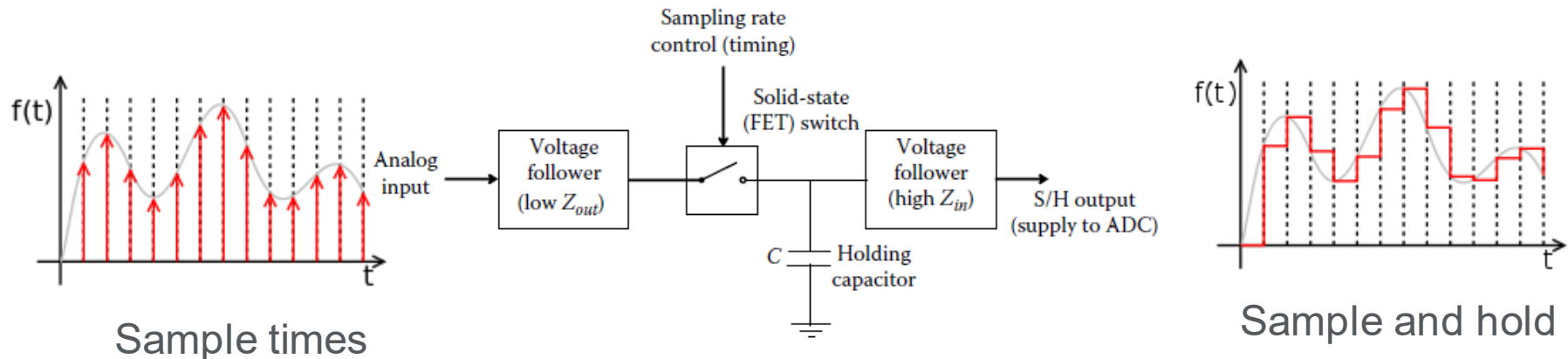

Z_{out} Voltage follower is used to provide low output impedance during charging of holding capacitor (Closing of FET switch).


Z_{in} voltage follower is used to provide high input impedance once the FET switch is open.

Flash A-D converters

  

Flash A-D converters



Vin= 5.5 Volts (From Analog input)

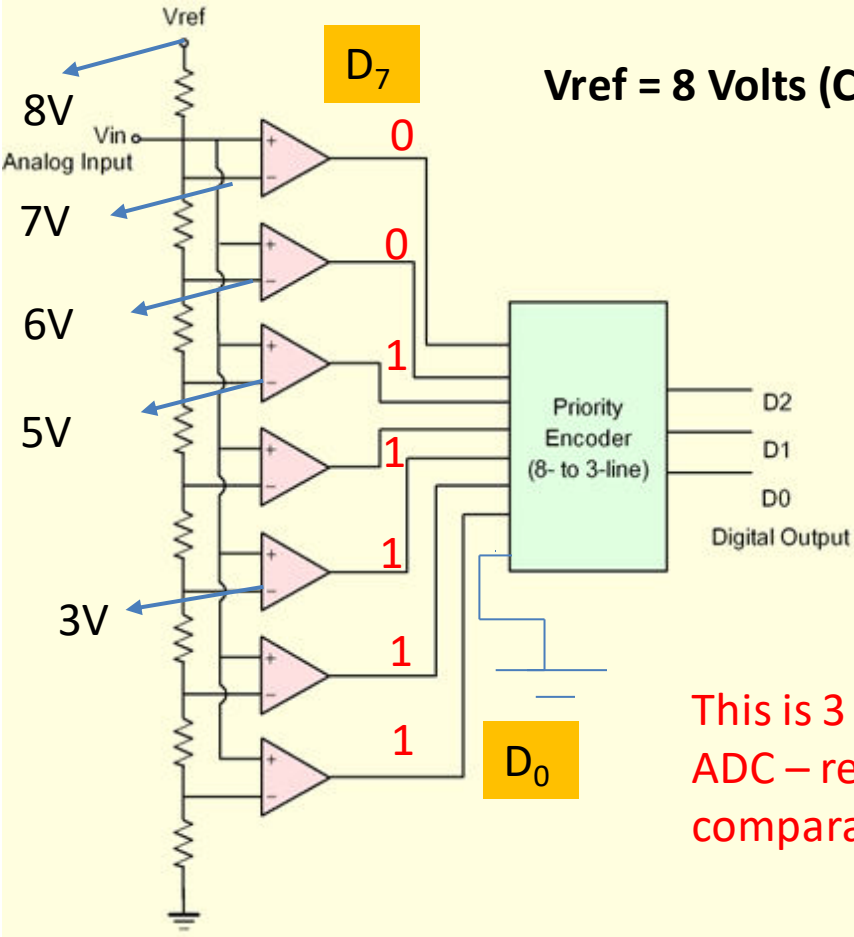

This is 3 bit Flash ADC – requiring 2^3-1 comparators.

Flash A-D converters

Our case is 0 0 1 1 1 1 1 1

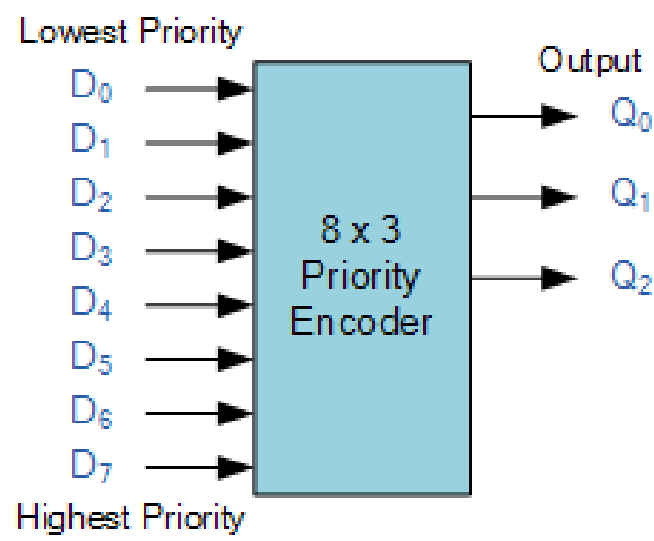 

| Inputs | | | | | | | | Outputs | | |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| D ₇ | D ₆ | D ₅ | D ₄ | D ₃ | D ₂ | D ₁ | D ₀ | Q ₂ | Q ₁ | Q ₀ |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | x | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 1 | x | x | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 1 | x | x | x | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | x | x | x | x | 1 | 0 | 0 |
| 0 | 0 | 1 | x | x | x | x | x | 1 | 0 | 1 |
| 0 | 1 | x | x | x | x | x | x | 1 | 1 | 0 |
| 1 | x | x | x | x | x | x | x | 1 | 1 | 1 |

X = dont care

Output 1 0 1 corresponds to 5V

Priority Encoders



MOTOROLA

10-LINE-TO-4-LINE AND 8-LINE-TO-3-LINE PRIORITY ENCODERS

The SN54/74LS147 and the SN54/74LS148 are Priority Encoders. They provide priority decoding of the inputs to ensure that only the highest order data line is encoded. Both devices have data inputs and outputs which are active at the low logic level.

The LS147 encodes nine data lines to four-line (8-4-2-1) BCD. The implied decimal zero condition does not require an input condition because zero is encoded when all nine data lines are at a high logic level.


The LS148 encodes eight data lines to three-line (4-2-1) binary (octal). By providing cascading circuitry (Enable Input EI and Enable Output EO) octal expansion is allowed without needing external circuitry.

The SN54/74LS748 is a proprietary Motorola part incorporating a built-in deglitcher network which minimizes glitches on the GS output. The glitch occurs on the negative going transition of the EI input when data inputs 0–7 are at logical ones.

**SN54/74LS147
SN54/74LS148
SN54/74LS748**


**10-LINE-TO-4-LINE
AND 8-LINE-TO-3-LINE
PRIORITY ENCODERS**

LOW POWER SCHOTTKY

 

**J SUFFIX
CERAMIC
CASE 620-09**

Successive approximation ADC

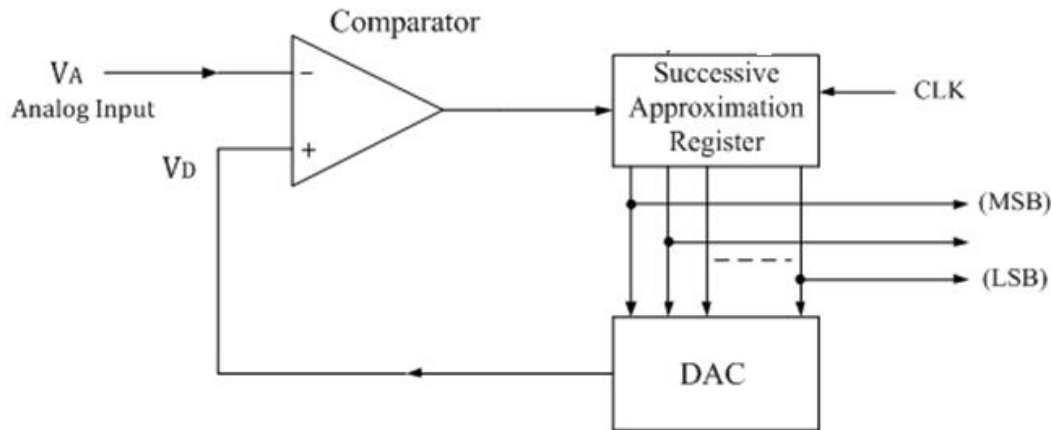

4 bit analysis


- Analog input is 3 Volts (V_A) - Say
- SAR generates 1 0 0 0
- DAC converts 1 0 0 0 to 8 Volts
- Compare it in comparator
- $8 > 3$, true, send next
- 0 1 0 0 (4 volts)
- $4 > 3$, true, send next
- 0 0 1 0 (2 volts)
- $2 > 3$, false hence, retain 0 0 **1** 0
- Send next 1 (LSB)
- 0 0 **1** 1
- Thus the digital O/P **0 0 1 1** of analog 3 Volts

n bit word takes n steps to make the comparison

If clock has frequency f , the time between pulses is $1/f$

Conversion time is n/f

Multiplexer

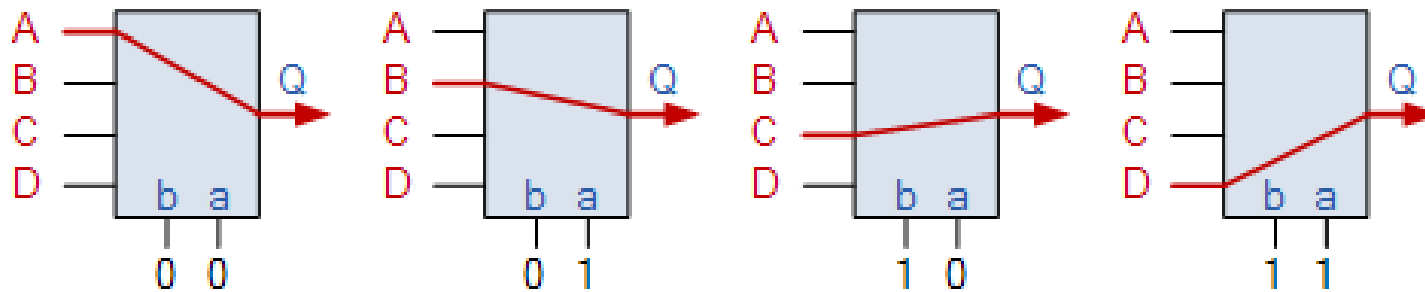

- Provides an output from just one of many input data
- Avoids separate ADC and microprocessor for each measurement



Parity bit concept for error detection

At **source**, The data 10101 is given the even parity bit of 1, resulting in the bit sequence 101011.

Detects loss of data

During transmission of data, Suppose 1**0**1011 becomes , say 1**1**1011, **receiver** will detect lack of even parity and nullifies the data.

Thank you